
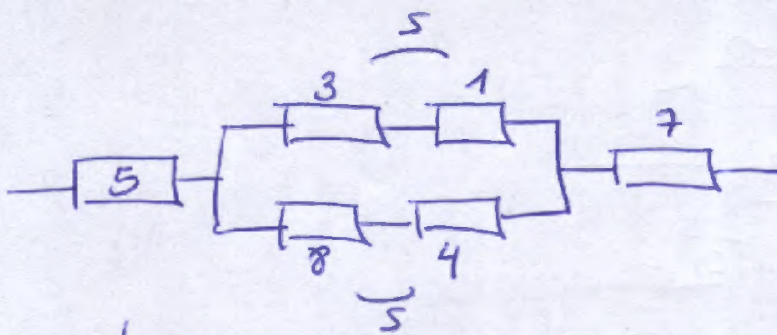



a)

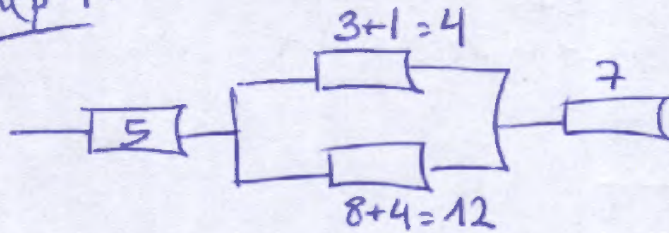

step 1:




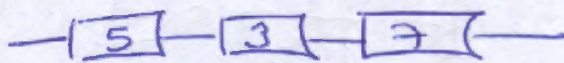step 2: $4 // 12$ $\frac{4 \cdot 12}{4 + 12} = \frac{48}{16} = 3$



step 3: $R_T = 5 + 3 + 7 = \underline{\underline{15 \Omega}}$


b)

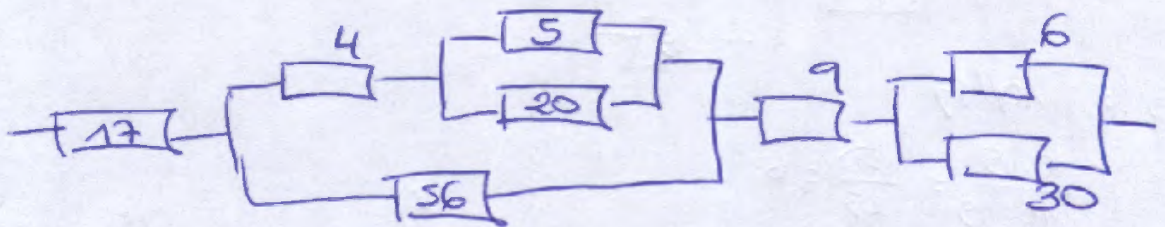

step 1 $5 // 20$ 2 $6 // 30$


$$\frac{5 \cdot 20}{5 + 20} = \frac{100}{25} = 4$$
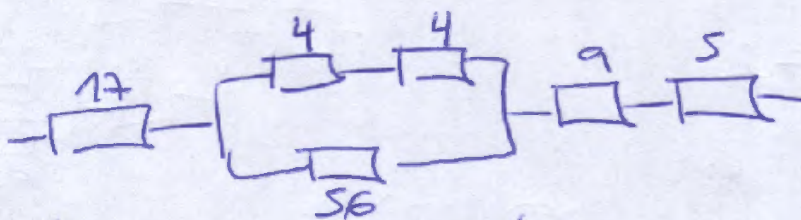
$$\frac{6 \cdot 30}{6 + 30} = \frac{180}{36} = 5$$




step 2 $4 + 4$ (series) $// 56$
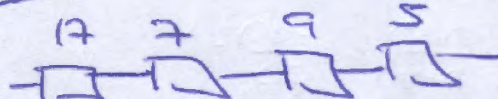
$$\frac{8 \cdot 56}{8 + 56} = \frac{448}{64} = 7$$




step 3: $R_T = 17 + 7 + 9 + 5 = 38 \Omega$

c)

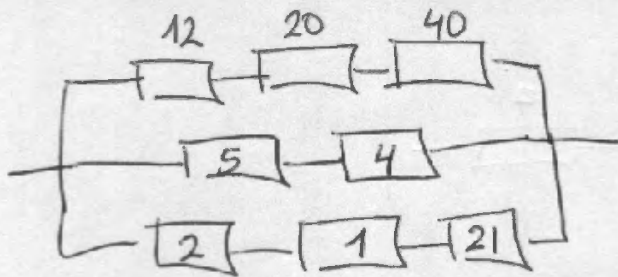

step 1: series

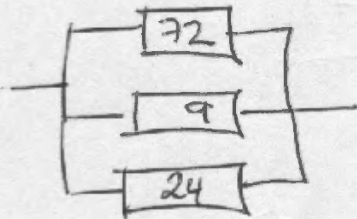
$$\begin{cases} 12+20+40 = 72 \\ 5+4 = 9 \\ 2+1+21 = 24 \end{cases}$$



step 2: $72 \parallel 9$ $R_{eq} = \frac{72 \cdot 9}{72+9} = 8$

step 3: $8 \parallel 24$ $R_T = \frac{8 \cdot 24}{8+24} = 6 \Omega$

d)

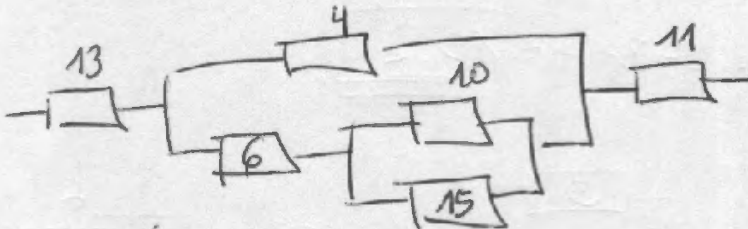

step 1: $10 \parallel 15$


$$\frac{10 \cdot 15}{10+15} = \frac{150}{25} = 6$$

step 2: $4 \parallel 6$ $= 4 \parallel 12$

$$\frac{4 \cdot 12}{4+12} = \frac{48}{16} = 3$$

step 3: $13+3+11 = 27 \Omega$

e)

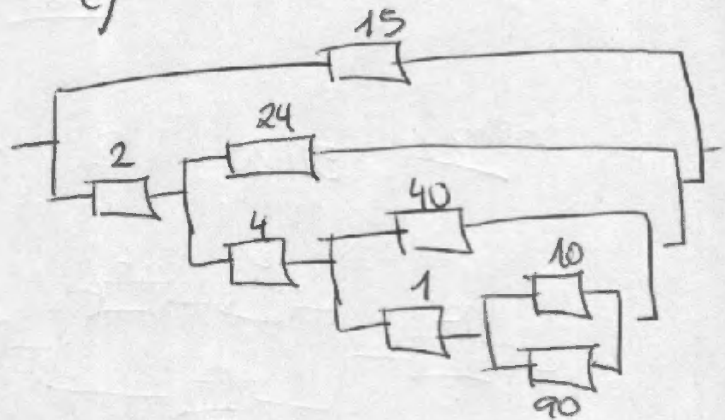

step 1

$$10 \parallel 90 = \frac{10 \cdot 90}{10+90} = \frac{900}{100} = 9$$

step 2

$$9 \parallel 4 = \frac{9 \cdot 4}{9+4} = \frac{36}{13} \approx 2.77$$

step 3

$$8+4 \parallel 24 = \frac{12 \cdot 24}{12+24} = 8$$

step 4

$$8+2 \parallel 15 = \frac{10 \cdot 15}{10+15} = \frac{150}{25} = 6 \Omega$$

~~27~~

$$\textcircled{1} \quad a) R_{\text{eq}} = R_1 + R_2 + R_3 = 5 + 10 + 7 = 22 \Omega$$

$$b) I = \frac{V}{R_{\text{eq}}} = \frac{110}{22} = 5 \text{ A.}$$

$$c) V_1 = I \cdot R_1 = 5 \cdot 5 = 25 \text{ V.}$$

$$V_2 = I \cdot R_2 = 5 \cdot 10 = 50 \text{ V.}$$

$$V_3 = I \cdot R_3 = 5 \cdot 7 = 35 \text{ V.}$$

$$\underline{110 \text{ V.}}$$

$$\textcircled{2} \quad a) R \quad V_3 = V_{\text{battery}} - V_1 - V_2 = 40 - 10 - 20 = 10 \text{ V.}$$

$$b) I = \frac{V_3}{R_3} = \frac{10}{2} = 5 \text{ A.}$$

$$c) R_2 = \frac{V_2}{I} = \frac{20}{5} = 4 \Omega$$

$$R_1 = \frac{V_1}{I} = \frac{10}{5} = 2 \Omega$$

$$\textcircled{3} \quad a) R_{\text{eq}} \quad \text{step 1: } R_1 // R_2 = R_{12} = \frac{4 \cdot 12}{4 + 12} = \frac{48}{16} = 3 \Omega$$

$$\text{step 2: } R_{12} // R_3 : R_T = \frac{3 \cdot 6}{3 + 6} = \frac{18}{9} = 2 \Omega.$$

$$b) I = \frac{V}{R_T} = \frac{12}{2} = 6 \text{ A.}$$


$$c) I_1 = \frac{V}{R_1} = \frac{12}{4} = 3 \text{ A.}$$

$$I_2 = \frac{V}{R_2} = \frac{12}{12} = 1 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{12}{6} = 2 \text{ A}$$

$$I_1 + I_2 + I_3 = I_T$$

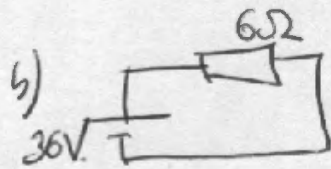④ a) Req. $R_a = R_1 + R_2 = 6 + 2 = 8 \Omega$
 $R_b = R_3 + R_4 = 20 + 4 = 24 \Omega$
 $R_{eq} = R_a // R_b = \frac{24 \cdot 8}{24 + 8} = \frac{192}{32} = 6 \Omega$



$I = \frac{36}{6} = 6 \text{ A.}$

c) $I_a = \frac{V}{R_a} = \frac{36}{8} = 4.5 \text{ A.}$
 $I_b = \frac{V}{R_b} = \frac{36}{24} = 1.5 \text{ A.}$
 $I_a + I_b = I_T$

d) $V_1 = I_a \cdot R_1 = 4.5 \cdot 6 = 27 \text{ V}$
 $V_2 = I_a \cdot R_2 = 4.5 \cdot 2 = 9 \text{ V.}$
 $V_1 + V_2 = V_{\text{battery}}$

$V_3 = I_b \cdot R_3 = 1.5 \cdot 20 = 30 \text{ V.}$
 $V_4 = I_b \cdot R_4 = 1.5 \cdot 4 = 6 \text{ V.}$
 $V_3 + V_4 = V_{\text{battery}}$

⑤ a) ~~$I_3 = I_T$~~ $I_3 = I_T - I_1 - I_2$
 $I_3 = 12 - 4 - 6 = 10 \text{ A.}$

b) $V_{\text{battery}} = V_{R_1} = V_{R_2} = V_{R_3}$
 $R_3 = \frac{V_{R_3}}{I_3} = \frac{2}{10} = 0.2 \Omega.$

c) $R_1 = \frac{V_{R_1}}{I_1} = \frac{2}{4} = 0.5 \Omega$
 $R_2 = \frac{V_{R_2}}{I_2} = \frac{2}{6} = 0.3 \Omega$


6) a) R_{eq}

$$R_a = R_1 // R_2 = \frac{3 \cdot 6}{3+6} = \frac{18}{9} = 2 \Omega$$

$$R_b = R_3 // R_4 = \frac{6 \cdot 12}{6+12} = \frac{72}{18} = 4 \Omega$$

$$R_{eq} = R_a + R_b = 2 + 4 = 6 \Omega$$

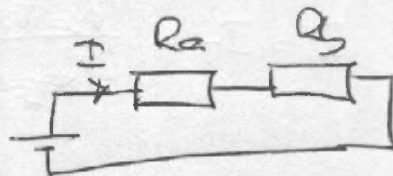b) $I = \frac{V}{R_T} = \frac{18}{6} = 3 \text{ A.}$



c) $V_1 = V_2 = R_a \cdot I = 2 \cdot 3 = 6 \text{ V.}$

$$V_3 = V_4 = R_b \cdot I = 4 \cdot 3 = 12 \text{ V.}$$

18V

d) $I_1 = \frac{V_a}{R_1} = \frac{6}{3} = 2 \text{ A}$
 $I_2 = \frac{V_a}{R_2} = \frac{6}{6} = 1 \text{ A}$ } $I_1 + I_2 = I$

$$I_3 = \frac{V_b}{R_3} = \frac{12}{6} = 2 \text{ A}$$

 $I_4 = \frac{V_b}{R_4} = \frac{12}{12} = 1 \text{ A.}$ } $I_3 + I_4 = I$